

Lab 9: Integrating Fetch and Decode

Jiasen Zhou, Jon Johnston

March 27, 2019

1 Executive Summary

The Executive Summary section should be a single concise paragraph that describes the following items. Please note that this should be a paragraph, not an itemized list like I have below. The list is just to tell you what I'm looking for...it is not there for you to fill it in on your lab report. See the Lab 1 Example Report.pdf on Canvas to see a good example of what I'm looking for.

2 Test Report


To verify operation of these module, this lab requires one test bench.

1. datapath

Figure 1: Expected Results of the datapath test.

	Instruction 1	Instruction 2	Instruction 3	Instruction 4	Instruction 5	Instruction 6	Instruction 7	Instruction 8	Instruction 9	Instruction 10
Instruction	LDUR X9, [X22, #64]	ADD X10, X19, X9	SUB X11, X20, X10	STUR X11, [X22, #96]	CBZ X11, -5	CBZ X9, 8	B 64	B -55	ORR X9, X10, X21	AND X9, X22, X10
Machine instruction (hex)	F84402C9	8B09020A	C80A028B	F80602CB	84FFFF6B	B4000109	34000040	17FFFFC9	AA150149	BA0A02C9
opcode (binary)	11111000010	10001011000	110001011000	11111000000	10110100	10110100	000101	000101	10101010000	10001010000
sign_extended_output (hex)	0000000000000040	0000000000000000	0000000000000000	0000000000000000	FFFFFFFFFFFFFFF8	0000000000000008	0000000000000040	000101	0000000000000000	0000000000000000
reg2_loc	0	0	0	1	1	1	0	0	0	0
branch	0	0	0	0	1	1	0	0	0	0
mem_read	1	0	0	0	0	0	0	0	0	0
mem_to_reg	1	0	0	0	0	0	0	0	0	0
alu_op	00	10	10	00	01	01	00	00	10	10
mem_write	0	0	0	1	0	0	0	0	0	0
alu_src	1	0	0	1	0	0	0	0	0	0
reg_write	1	1	1	0	0	0	0	0	1	1
uncondbranch	0	0	0	0	0	0	1	1	0	0
write_data (decimal)	20	30	0	X	X	X	X	X	30	16
read_data1 (decimal)	10	10	30	10	X	X	X	X	30	16
read_data2 (decimal)	X	20	30	0	0	20	X	X	0	30
branch_target	X	4	8	396	-4	52	280	-192	32	36
alu_result	80	30	0	112	0	20	X	X	30	16
zero	0	0	1	0	1	0	0	0	0	0

Figure 2: Timing diagram for the datapath test.

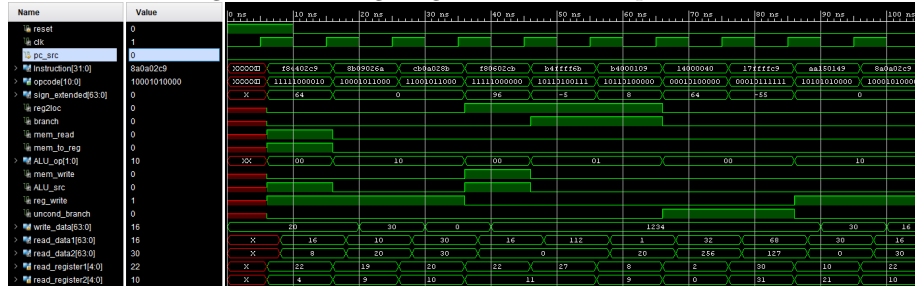

3 Code Appendix

Listing 1: Verilog code for testing the datapath.

```

`include "definitions.vh"

module datapath;

    reg reset, pc_src;
    wire [WORD-1:0] branch_target, cur_pc;
    wire [INSTR_LEN-1:0] Instruction;
    reg [WORD-1:0] write_data;
    wire uncond_branch, branch, mem_read, mem_to_reg, mem_write, ALU_src;
    wire clk, clkplus1, clkplus2, clkplus3, clkplus4, clkplus5, clkplus6;
    wire [1:0] ALU_op;
    wire [WORD-1:0] read_data1, read_data2, sign_extended;
    wire [WORD-1:0] alu_result;
    wire zero;

    //fetch takes 2ns to complete. So clk and clkplus1 are used in fetch

```

```

oscillator r_clk(.clk(clk));
delay ClkPlus1(.a(clk), .a_delayed(clkplus1));
delay #(.DELAYAMT(2)) ClkPlus2(.a(clk), .a_delayed(clkplus2));
delay #(.DELAYAMT(3)) ClkPlus3(.a(clk), .a_delayed(clkplus3));
delay #(.DELAYAMT(4)) ClkPlus4(.a(clk), .a_delayed(clkplus4));
delay #(.DELAYAMT(5)) ClkPlus5(.a(clk), .a_delayed(clkplus5));
delay #(.DELAYAMT(6)) ClkPlus6(.a(clk), .a_delayed(clkplus6));


fetch iFetch(.clk(clk),
              .reset(reset),
              .branch_target(branch_target),
              .pc_src(pc_src),
              .instruction(Instruction),
              .cur_pc(cur_pc));

iDecode decode_mod(
    .write_data(write_data),
    .Instruction(Instruction),
    .uncond_branch(uncond_branch),
    .branch(branch),
    .mem_read(mem_read),
    .mem_to_reg(mem_to_reg),
    .mem_write(mem_write),
    .ALU_src(ALU_src),
    .read_clk(clkplus3),
    .write_clk(clkplus6),
    .ALU_op(ALU_op),
    .read_data1(read_data1),
    .read_data2(read_data2),
    .sign_extended(sign_extended));

iExecute execute_mod(
    .pc_in(cur_pc),
    .read_data1(read_data1),
    .read_data2(read_data2),
    .sign_extend(sign_extended),
    .opcode(Instruction[31:21]),
    .alu_op(ALU_op),
    .alu_src(ALU_src),
    .alu_result(alu_result),
    .zero(zero),
    .branch_target(branch_target));

initial
begin
    reset = 1;

```

```
        pc_src= 0;
        write_data = 20;#10;
        reset = 0;
        write_data = 20;#10;
        write_data = 30;#10;
        write_data = 0;#10;
        write_data = 1234; #50;
        write_data = 30; #10;
        write_data = 16; #6;
    $finish;
end
endmodule
```