

Lab 12: Pipeline Fetch and Decode

Jiasen Zhou, Jon Johnston

April 27, 2019

1 Executive Summary

Fill.

2 Test Report

To verify operation of these modules, this lab required one test bench.


1. Pipeline Test Bench

2.1 Pipeline Test Bench

The Pipeline Test Bench contains:

1. Inputs
 - (a) Fill.
2. Outputs
 - (a) Fill.

Figure 1: Timing Diagram of the Pipeline test.

 

3 Code Appendix

Listing 1: Verilog code for testing the pipelined datapath

```

#include "definitions.vh"

module pipeline;

    reg reset;
    wire [INSTR_LEN-1:0] instruction_if;
    wire uncond_branch_id, branch_id,
        mem_read_id, mem_to_reg_id,
        mem_write_id, reg_write_id,
        ALU_src_id, clk;
    // Future
    /* zero_ie, pc_src, uncond_branch_ie,
       branch_ie, mem_read_ie, mem_to_reg_ie,
       mem_to_reg_im, mem_write_ie, reg_write_ie,
       reg_write_im, reg_write_iw, */
    wire [1:0] ALU_op_id;
    wire [4:0] write_register_id;
    // Future
    /* write_register_ie, write_register_im,

```

```

        write_register_iw*/
wire [WORD-1:0]
    cur_pc_if, cur_pc_id,
    read_data1_id,
    read_data2_id,
    sign_extended_output_id;
    // Future
    /* branch_target, cur_pc_ie, cur_pc_im,
       read_data_im, read_data2_ie, write_data_iw,
       alu_result_ie*/
wire [10:0] opcode_id;

// Temporary Registers for Simulation
reg pc_src, uncond_branch_ie, branch_ie,
    mem_read_ie, mem_to_reg_ie, mem_write_ie,
    reg_write_ie, reg_write_iw;
reg [4:0] write_register_iw;
reg [WORD-1:0] branch_target, cur_pc_ie,
    read_data2_ie, write_data_iw;

// Base Clock
oscillator r_clk(.clk(clk));

// Fetch Stage
fetch fetch_mod(
    .clk(clk),
    .reset(reset),
    .branch_target(branch_target),
    .pc_src(pc_src),
    .instruction_if(instruction_if),
    .cur_pc_if(cur_pc_if));

// Decode Stage
iDecode decode_mod(
    .cur_pc_if(cur_pc_if),
    .cur_pc_id(cur_pc_id),
    .write_data_iw(write_data_iw),
    .write_register_iw(write_register_iw),
    .write_register_id(write_register_id),
    .reg_write_iw(reg_write_iw),
    .reg_write_id(reg_write_id),
    .instruction_if(instruction_if),
    .uncond_branch_id(uncond_branch_id),
    .branch_id(branch_id),
    .mem_read_id(mem_read_id),
    .mem_to_reg_id(mem_to_reg_id),

```

```

        .mem_write_id(mem_write_id),
        .ALU_src_id(ALU_src_id),
        .write_clk(clk),
        .ALU_op_id(ALU_op_id),
        .read_data1_id(read_data1_id),
        .read_data2_id(read_data2_id),
        .sign_extended_output_id(sign_extended_output_id),
        .opcode_id(opcode_id));

// iExecute Buffer Simulation
always @(posedge clk)
begin
    uncond_branch_ie <= uncond_branch_id;
    branch_ie <= branch_id;
    mem_read_ie <= mem_read_id;
    mem_to_reg_ie <= mem_to_reg_id;
    mem_write_ie <= mem_write_id;
    reg_write_ie <= reg_write_id;
    cur_pc_ie <= cur_pc_id;
    read_data2_ie <= read_data2_id;
end

// Future Modules
// iExecute execute_mod(
//     .pc_in(cur_pc),
//     .read_data1(read_data1),
//     .read_data2(read_data2),
//     .sign_extend(sign_extended_output_id),
//     .opcode(opcode_id),
//     .alu_op(ALU_op),
//     .alu_src(ALU_src),
//     .alu_result(alu_result),
//     .zero(zero),
//     .branch_target(branch_target));

// iMemory memory_mod(
//     .im_clk(clk),
//     .alu_result(alu_result),
//     .read_data2(read_data2),
//     .mem_read(mem_read),
//     .mem_write(mem_write),
//     .zero(zero),
//     .branch(branch),
//     .uncondbranch(uncond_branch),
//     .read_data(read_data),
//     .pc_src(pc_src));

```

```
//      iWrite_back writeback_m(  
//          .read_data(read_data),  
//          .alu_result(alu_result),  
//          .MemtoReg(mem_to_reg),  
//          .write_data(write_data));  
  
initial  
    begin  
        reset = 1;  
        pc_src = 0;  
        branch_target = 0;  
        reg_write_iw = 0;  
        write_register_iw = 0;  
        write_data_iw = 0; #5  
        reset = 0; #40  
    $finish;  
    end  
  
endmodule
```